

Electronics Technology Fundamentals



Kapittel 18
Grunnleggende diodekoplinger
Basic Diode Circuits
Revidert versjon 13 feb. 2007 T.Lindem

18.1 Likerettere

- **Likeretter** – en diodekrets som omformer en AC til pulserende DC
- **Filter** – en krets som reduserer variasjonene i spenningen ut fra en likeretter
- **Voltage Regulator** – **Spenningsregulator** – krets som opprettholder konstant spenninga ut (spenningen holdes konstant selv om belastningen endres)


18.1 Halvbølge likeretter

■ Likerettere (fortsatt)

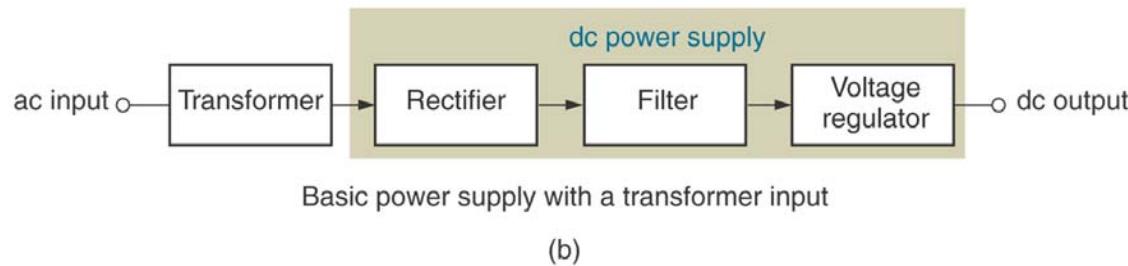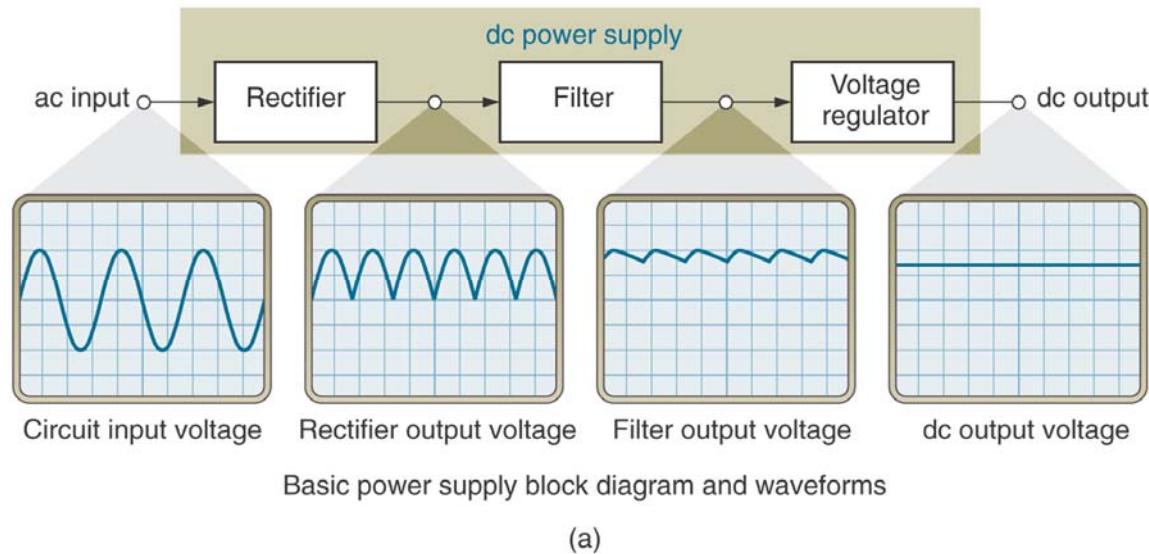


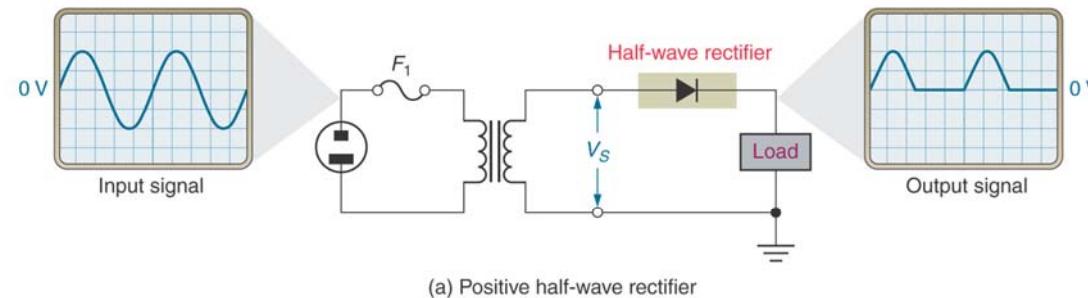18.1 Halvbølge likeretter

- Halvbølge likeretter – en diode er plassert i serie mellom en transformator og lasten (mottakerkretsen).
 - Positiv halvbølge likeretter – leverer en serie positive pulser
 - Negativ halvbølge likeretter – leverer en serie negative pulser



(a) Positive half-wave rectifier

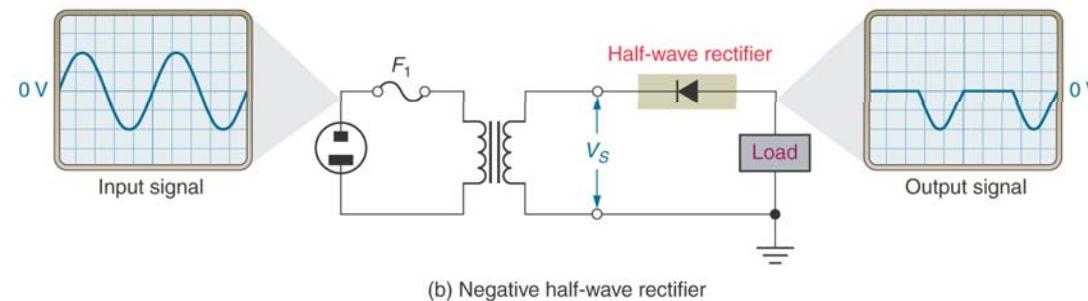

(b) Negative half-wave rectifier


18.1 Halvbølge likeretter

Half-Wave Rectifiers


Rectifier type:

Positive half-wave

Schematic diagram:

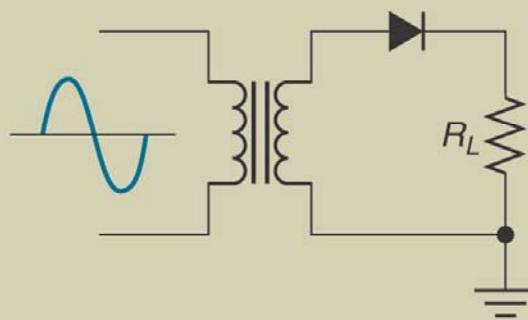

Negative half-wave

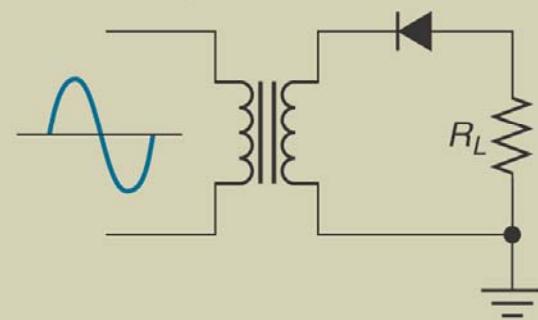

Circuit recognition:

The diode points toward the load (R_L).

When the diode conducts:

During the *positive* half-cycle of the input (V_S).

The diode points toward the source.


During the *negative* half-cycle of the input (V_S).

Resulting output waveform:



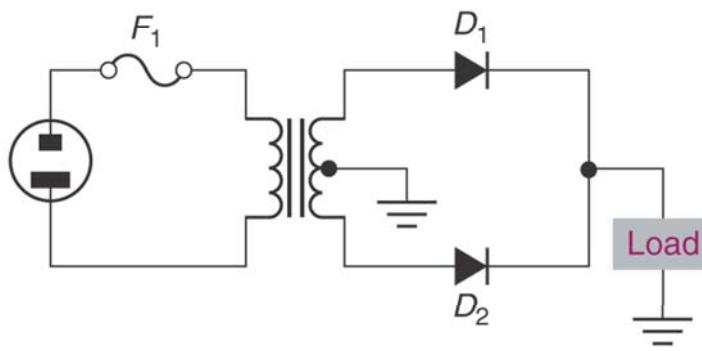
18.2 Helbølge likeretter

- Helbølge likeretter – består av to dioder som er forbundet til en sentertappet transformator



A full-wave rectifier

(a)

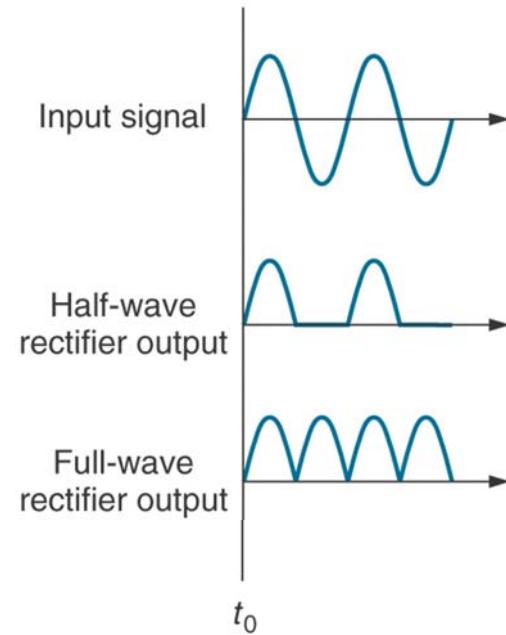


Typical rectifier waveforms


(b)

18.2 “Full-Wave” - Helbølge likeretter

■ Basic Circuit Operation

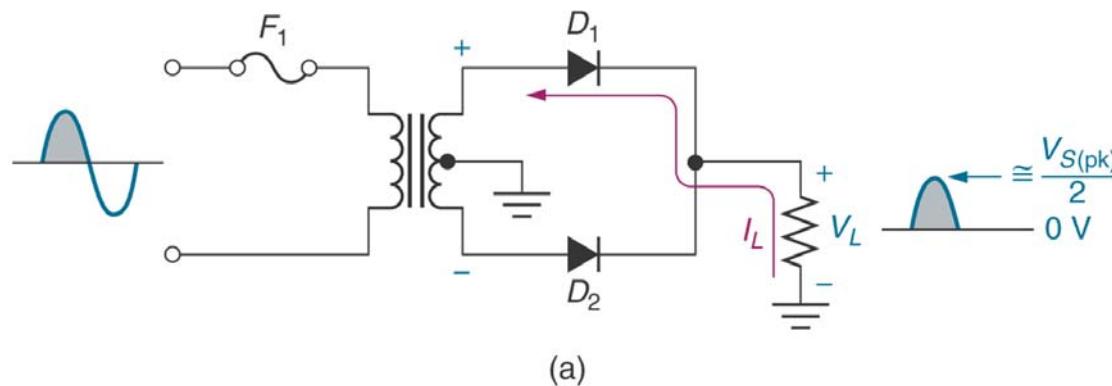


(a)

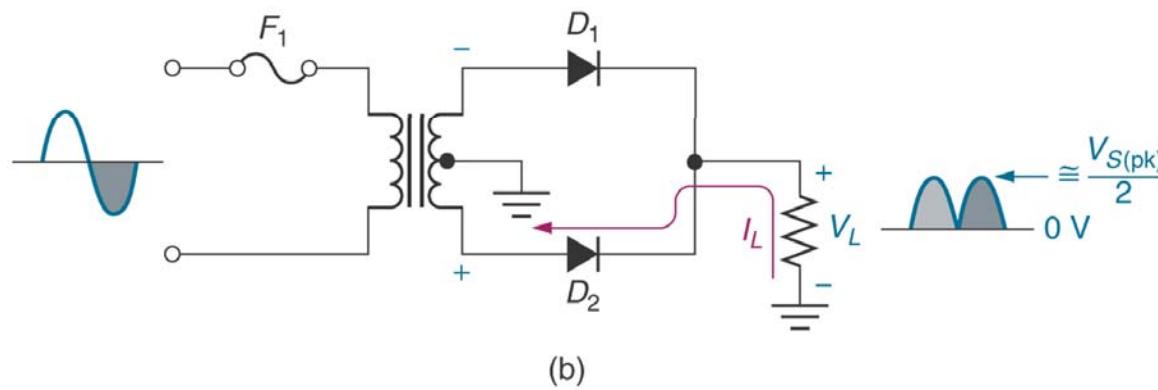

(b)

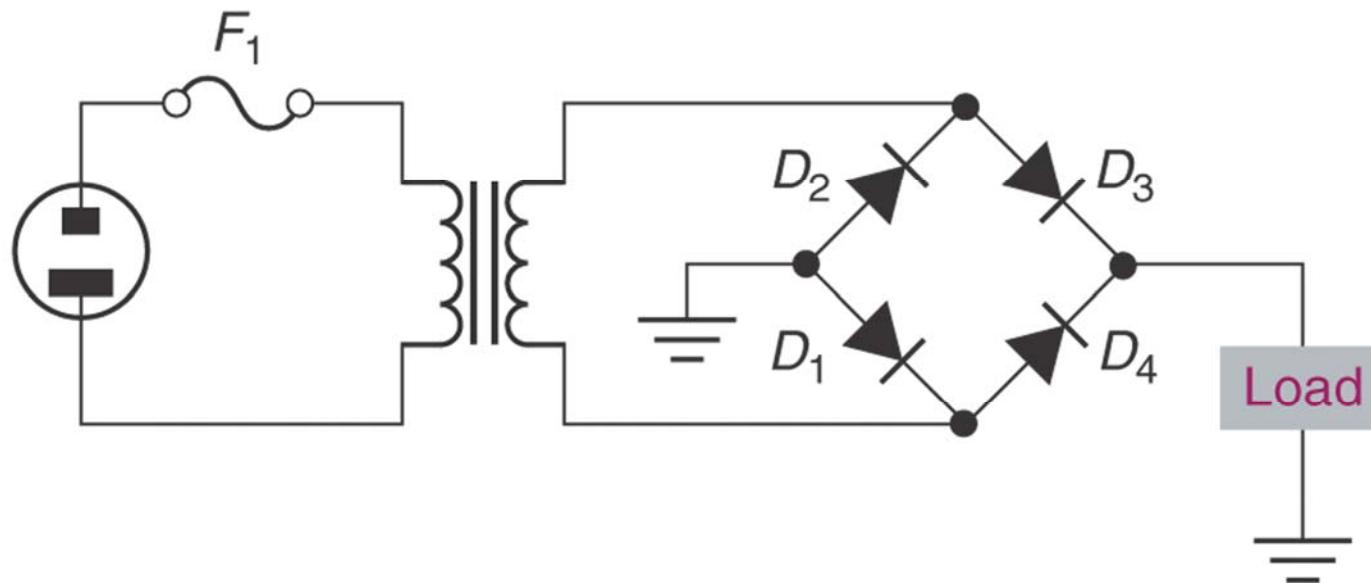
18.3 “Full-Wave” - Helbølge likeretter

- Helbølge likeretter – den mest benyttede likeretter
 - Trenger ikke sentertappet transformator




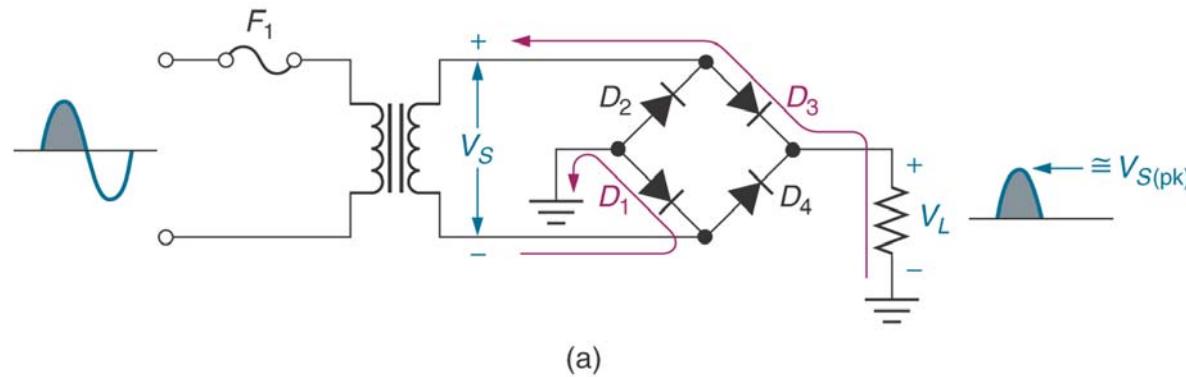18.3 “Full-Wave” - Helbølge likeretter

- Circuit Operation – conduction alternates between two diode pairs






(a)

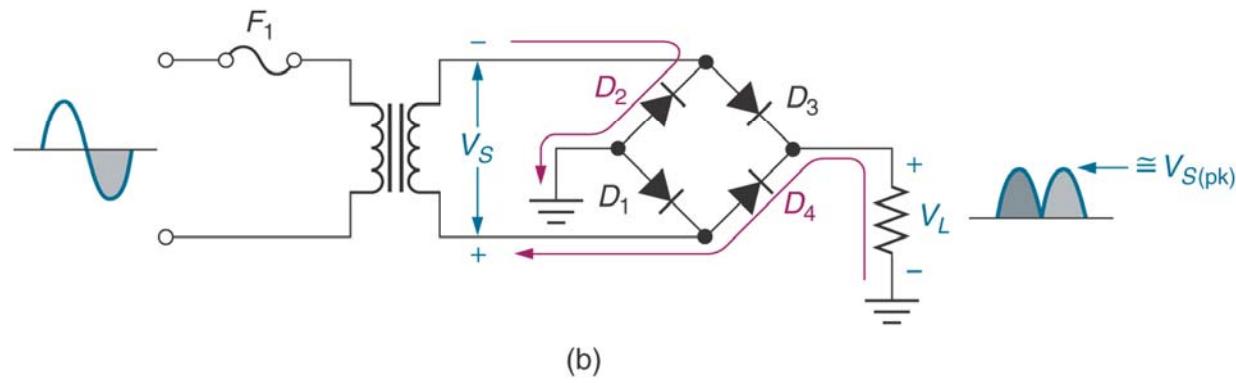

(b)


18.3 “Full-Wave” - Helbølge likeretter

Rectifiers: A Comparison

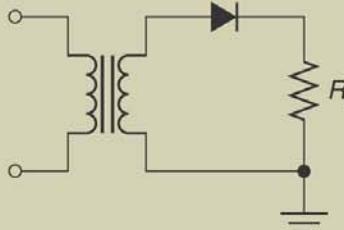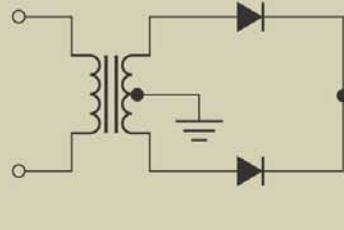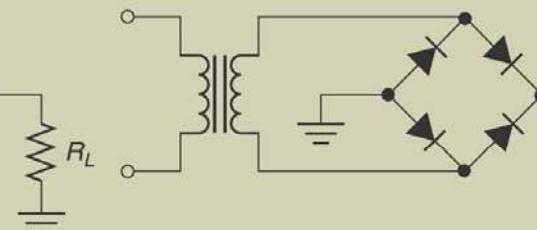Rectifier type:	Half-wave	Full-wave	Bridge
Schematic diagram:			
Typical output waveform:			
Peak load voltage:	$V_{S(\text{pk})} - 0.7 \text{ V}$	$\frac{V_{S(\text{pk})}}{2} - 0.7 \text{ V}$	$V_{S(\text{pk})} - 1.4 \text{ V}$
dc load voltage (V_{ave}):	$\frac{V_{L(\text{pk})}}{\pi}$	$\frac{2V_{L(\text{pk})}}{\pi}$	$\frac{2V_{L(\text{pk})}}{\pi}$
dc load current (I_{ave}):	$\frac{V_{\text{ave}}}{R_L}$	$\frac{V_{\text{ave}}}{R_L}$	$\frac{V_{\text{ave}}}{R_L}$
PIV:	Equal to $V_{S(\text{pk})}$	$V_{S(\text{pk})} - 0.7 \text{ V}$	$V_{S(\text{pk})} - 0.7 \text{ V}$

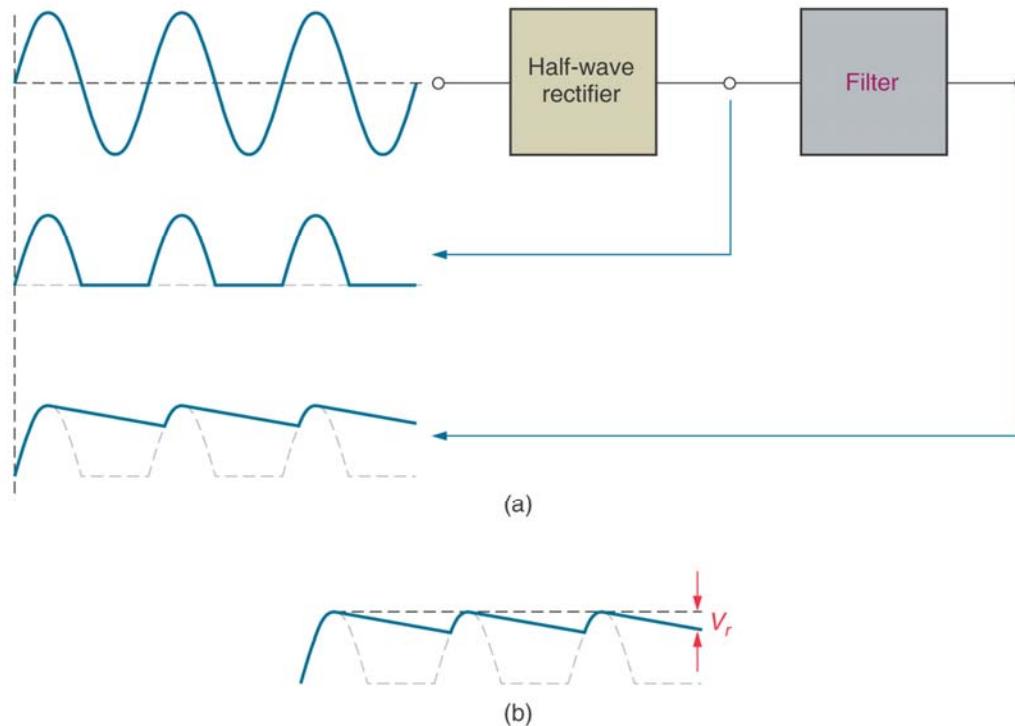
18.4 Likeretter med filter

- Power Supply Filter – en krets som reduserer variasjonene i DC spenningen ut fra likeretteren
 - Rippelspanning (V_R) – variasjonen i utgangs-spenningen (V_{PP})



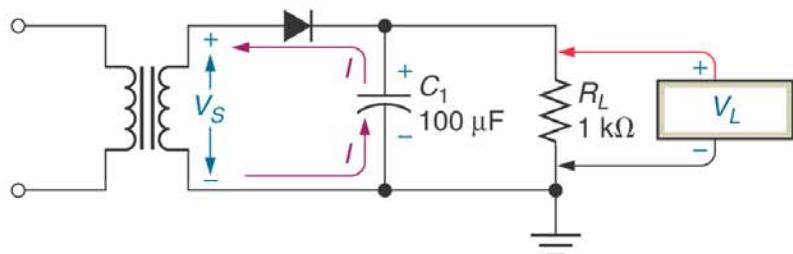
18.4 Likeretter med filter

- Basic Capacitive Filter – en kondensator er koplet i parallell med “lasten”



Charge circuit

(a)

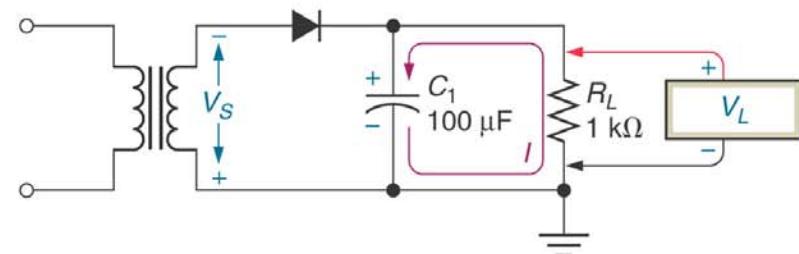

Discharge circuit

(b)

C_F constant

$R_L = 500 \Omega$

$R_L = 1 \text{ k}\Omega$

$R_L = 1.5 \text{ k}\Omega$

R_L constant

$C_F = 150 \mu\text{F}$



$C_F = 300 \mu\text{F}$

$C_F = 470 \mu\text{F}$

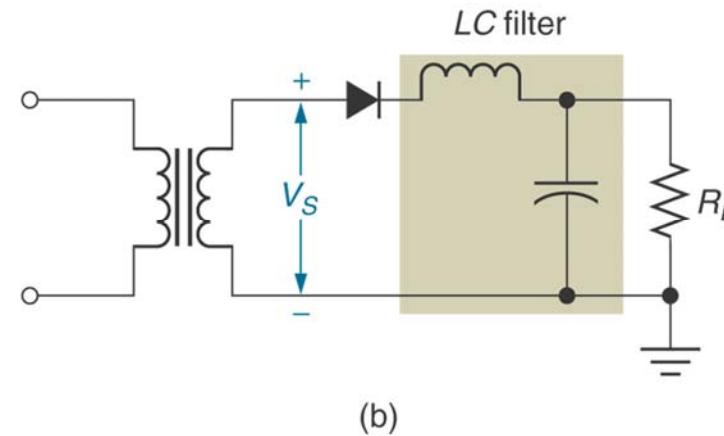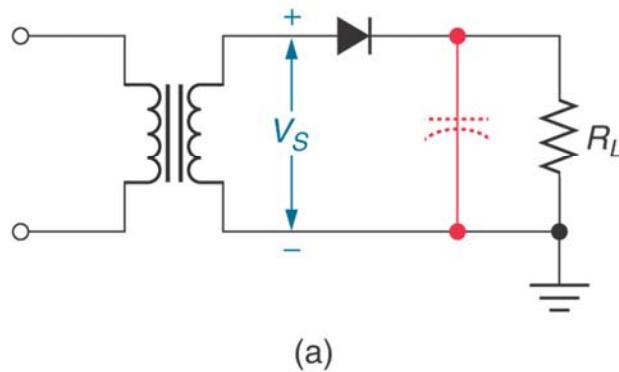18.4 Likeretter med filter


■ Surge Current

- At the first instant when a power supply is turned on, the discharged capacitor acts as a short circuit
- Rectifier current limited by:
 - Winding resistance of the transformer secondary
 - Bulk resistance of the diode
- Surge current can be limited by using *LC* / *RC* filter




18.4 Filtered Rectifiers – P11


■ Other Filter Types

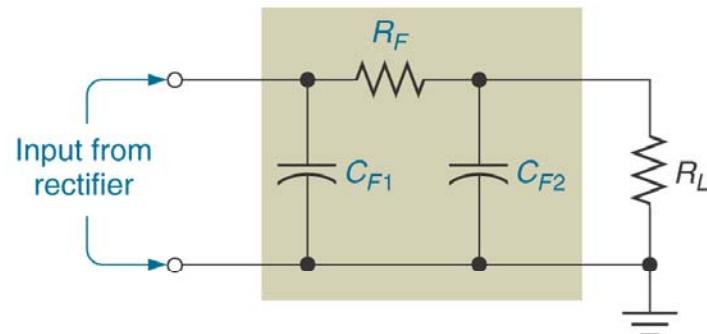

(a) *RC π filter*

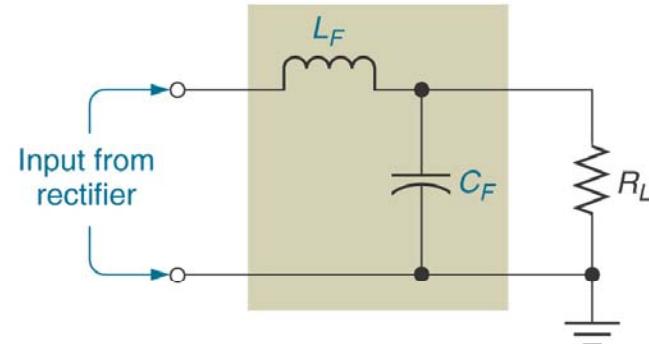

(b) *LC filter*

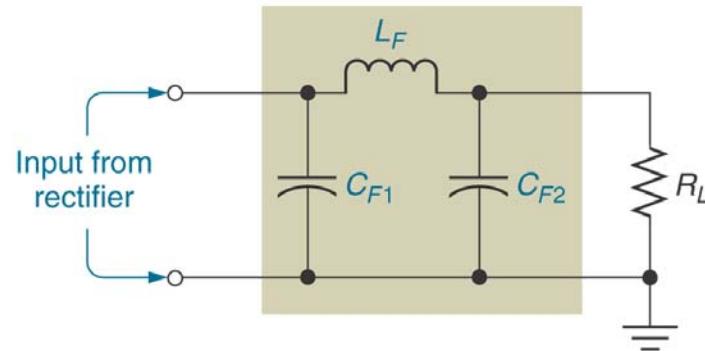


(c) *LC π filter*

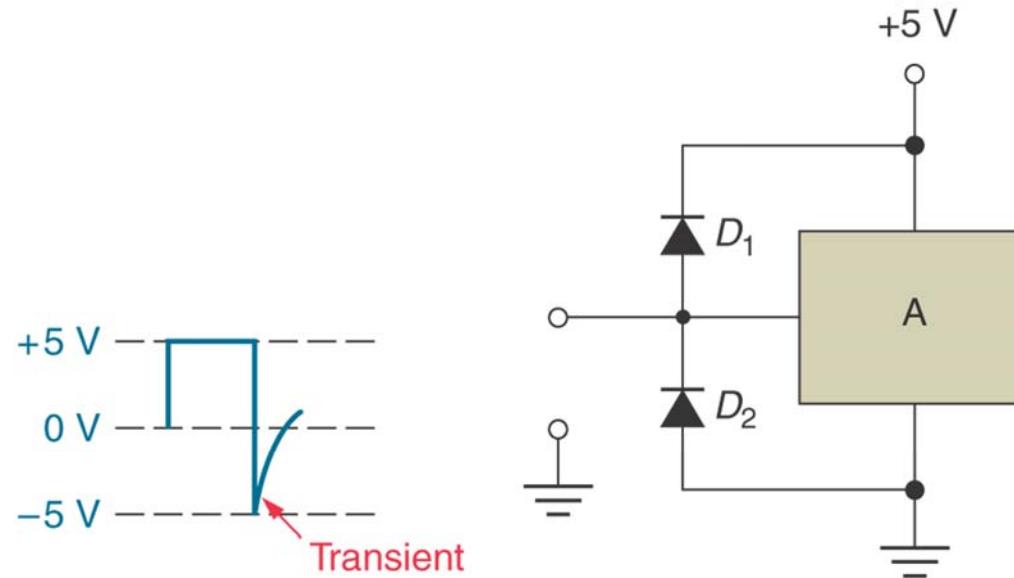18.5 Klippere


■ Transient beskyttelse

- ❑ Transient – en meget rask endring i enten strøm eller spenning – Kan ødelegge halvlederkomponenter. Forekommer ofte som elektrostatisk utladning når man berører komponenter. Har du klær av syntetisk materiale kan du fort ”lades opp” til spenninger på over 1000 volt. Det er viktig at du er ”jordet” når du behandler transistorer og integrerte kretser !
- ❑ Mange kretser må beskyttes mot overspenninger – til dette brukes diode ”klippere”. Diode D_1 leder hvis input-signalet overstiger +5 volt --- D_2 leder hvis input-signalet blir lavere enn -0,7 volt




18.7 Spenningsdoblere (Voltage Multipliers)

■ Halvbølge “Voltage Doublers”

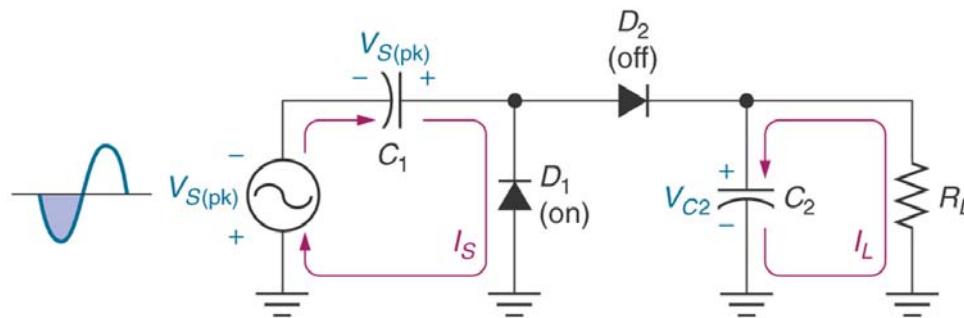

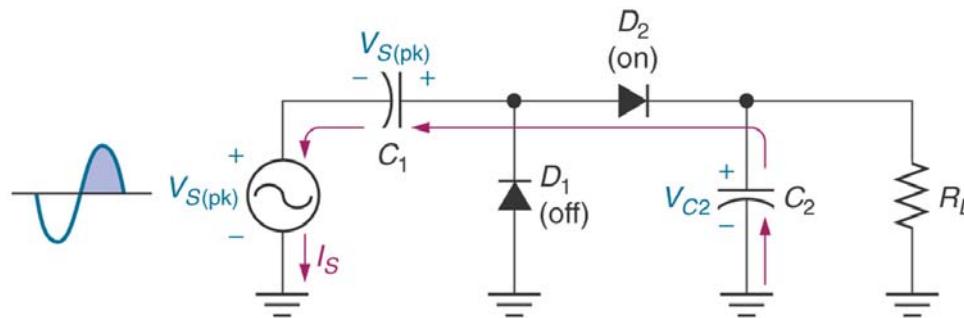
(a) C_1 charges and C_2 discharges during the negative alternation of the input.



(b) The source and C_1 charge C_2 during the positive alternation of the input.


18.7 Voltage Multipliers – P3

■ Half-Wave Voltage Doublers (Continued)

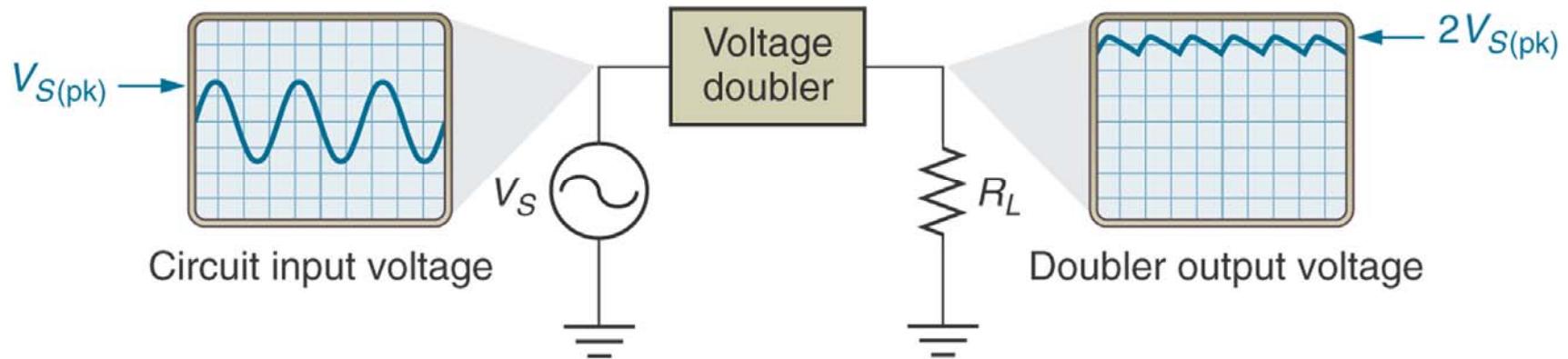


18.7 Voltage Multipliers – P4


■ Helbølge spenningsdoblere / tripler

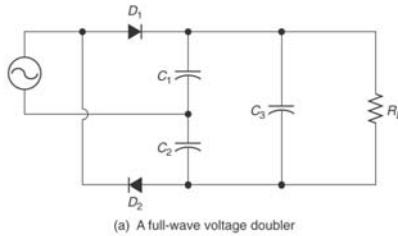


(a) A full-wave voltage doubler

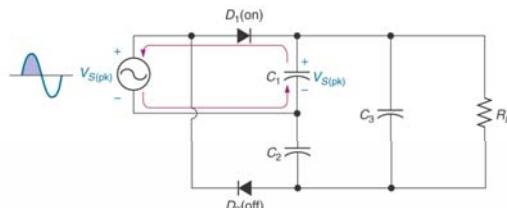

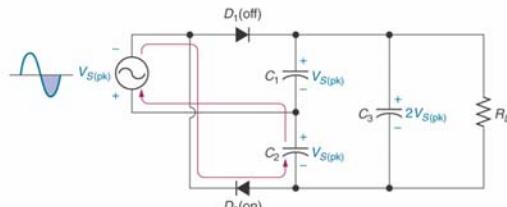
(b) C_1 is charged (via D_1) during the positive alternation of the input cycle.



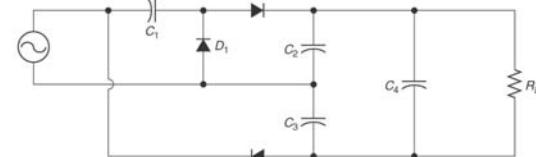
(c) C_2 is charged (via D_2) during the negative alternation of the input cycle.



(a) A voltage tripler

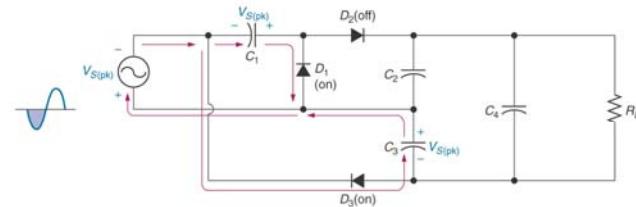

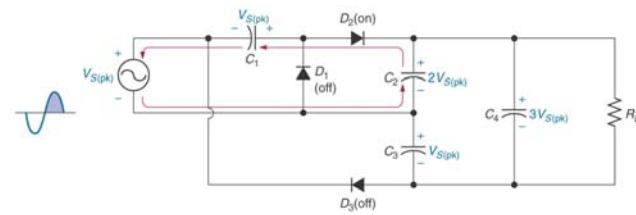(b) C_1 and C_3 are charged during the negative alternation of the input cycle.



(c) C_2 is charged during the positive alternation of the input cycle.

18.7 Voltage Multipliers – P6

■ Voltage Quadrupler

